
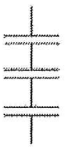


Ch. 29 (capacitors) and Ch. 31 (circuits) Conceptual Questions


1. Each capacitor in the circuits below has a capacitance of C . What is the equivalent capacitance of each group of capacitors?

a. $\frac{1}{C_{TOT}} = \frac{1}{C} + \frac{1}{C}$
 $\frac{2}{C} = \frac{1}{C_{TOT}}$
 $C_{eq} = \frac{C}{2}$

b.  $C_{eq} = 2C$ $C+C$


c. $\frac{1}{C} + \frac{1}{C} + \frac{1}{C} = \frac{1}{C_{TOT}}$
 $\frac{3}{C} = \frac{1}{C_{TOT}}$
 $C_{eq} = \frac{C}{3}$


d.  $C_{eq} = 3C$ $C+C+C$

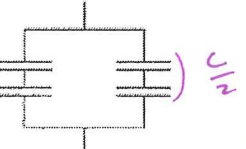
e. $\frac{C}{2} (\text{parallel}) \frac{C}{2}$
 $\frac{C}{2} + \frac{C}{2} = C_{TOT}$
 $C_{eq} = C$


f. $2C (\text{parallel}) \frac{2C}{5}$ $\frac{1}{C} + \frac{1}{2C} + \frac{1}{C}$
 $\frac{5}{2C} = \frac{1}{C_{TOT}}$
 $C_{eq} = \frac{2C}{5}$

2. Rank in order, from largest to smallest, the equivalent capacitance (C_{eq}) of each of the four groups of capacitors.

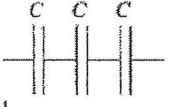1.  $\frac{C}{3}$

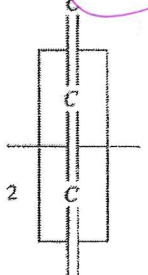2.  $3C$

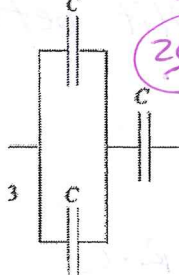
3.  $\frac{1}{2C} + \frac{1}{C} = \frac{1}{C_{TOT}}$
 $\frac{2C}{3}$

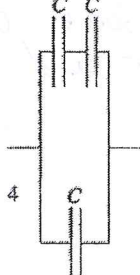4.  $\frac{C}{2} + C = \frac{3C}{2}$

$2 > 4 > 3 > 1$

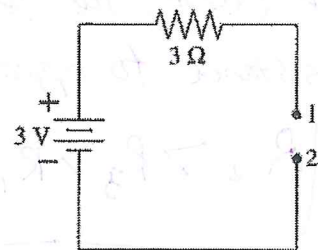3. The wire is broken on the right side of the circuit. What is the potential difference (ΔV_{12}) between points 1 and 2? Explain your reasoning.


3 Volts. No current flowing so no ΔV across resistor. Via the loop rule there must be a ΔV of 3V since $\Delta V_{loop} = 0$



4. The circuit to the right has two resistors, with $R_1 > R_2$. Which of the two resistors dissipates the larger amount of power? Explain your logic.

$P = I^2 R$; I is the same in a series circuit, so
 or
 $P = V \cdot I$
 or
 $P = \frac{V^2}{R}$


$P_1 > P_2$

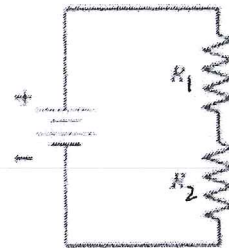

5. The circuit to the right also has two resistors, with $R_1 > R_2$. Which of the two resistors dissipates the larger amount of power? Explain your logic.


$P = \frac{V^2}{R}$ Voltage is the same across both, so since $R_1 > R_2$

$P_2 > P_1$

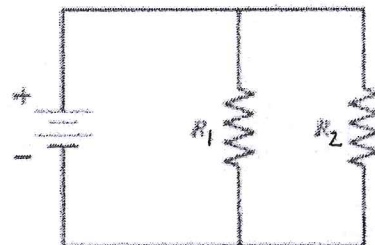

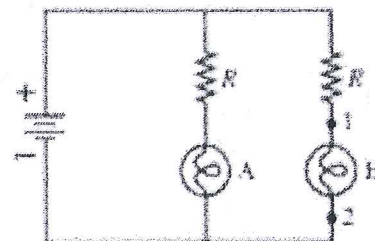6. Bulbs A and B in the diagram to the right are identical, and both are glowing. Bulb B is then removed from its socket. Does the potential difference ΔV_{12} between points 1 and 2 increase, decrease, stay the same, or become zero? Explain.

ΔV_{12} actually increases. Since no current flows in that branch, all the ΔV is now between 1 & 2, whereas before some was split between the resistor and Bulb B.



7. The diagram to the right shows voltage as a function of time of a capacitor as it is discharged (separately) through three different resistors. Rank, in order from largest to smallest, the values of the resistances R_1 to R_3 .

$\tau = R \cdot C$

Same capacitor, so the steeper the curve, the less the resistance to oppose discharging.

So... $R_2 > R_3 > R_1$

